University of Engineering and Technology, Peshawar

Department of Computer Systems Engineering. <u>Course Lab: CSE-308 Digital System Design</u>

Zubair Khan
Section
Batch
Submitted to



19 PWCSE 1797 A 21 (Spring_2022) Engr. Madiha Sher

LAB # 7 TITLE

DESIGN OF A LIGHT SWITCH


Objective:


Build a light switch controller such that when the push button is pressed the light if "off" turns "on" and if "on" turns "off".

Block Diagram:


The top level block diagram is shown in the following figure. The second diagram is a more detailed view of the top level diagram. Synchronizer circuit is used to avoid the metastability problem which arises when synchronous digital system are fed with an asynchronous input. The level to pulse converter is there to convert level input from a push button into a pulse that is highfor onlyone clock cycle. The switch button FSM is actually implementing the state machine for the requirement i-e when the push button is pressed the light if "off" turns "on" and if "on" turns "off".

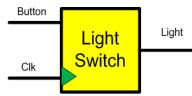I/O connection: Connect the button input to a push button on the S3BOARD and light output to LED.




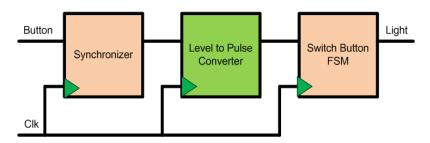


Synchronizer Circuit:

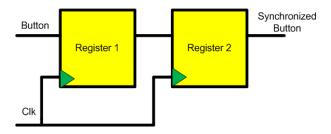

Level to Pulse FSM:

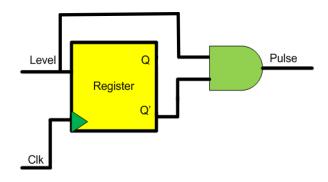

Switch Button FSM:

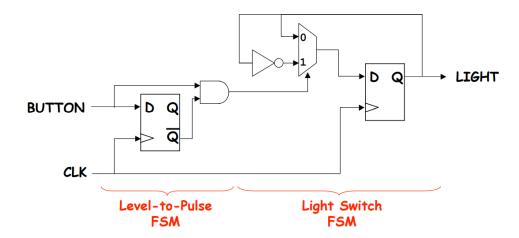

CODE:

```
module task2(clk,rst,in,out,pulse);
input clk,rst,in;
output
out,pulse;
wire synin, CLK_1hz;
CLOCK_Divider CD1(clk,rst,CLK_1hz);
synchron ss2(in,CLK_1hz,rst,synin); task1
t1(clk,rst,synin,pulse);
parameter
s0=0;parameter
s1=1;
reg state, next_state,out;
always @(posedge CLK_1hz)
begin
        if(~rst)
               begin
                       state=s0;
               end
        else
               state=next_state;
end
always @(*)
begin
        case(state)
               s0:
               begin
                       if(pulse==0)
                       begin
                               next_state=s0
                               ;out=0;
                               end
                       else
                       begin
                               next_state=s1
                               ;out=1;
                               end
                end
               s1:
               begin
                       if(pulse==1)
                       begin
                               next_state=s0
                               ;out=0;
                       end
                       else
                       begin
```

```
out=1;
                       end
               end
       endcas
end
endmodule
//designing the pulse
generatormodule
task1(clk,rst,in,out); input clk,
rst,in;
output out;
wire synin, CLK_1hz;
CLOCK_Divider CD(clk,rst,CLK_1hz);
synchron ss1(in,CLK_1hz,rst,synin);
parameter
s0=0;parameter
s1=1;
reg state, next_state,out;
always @(posedge CLK_1hz)
begin
       if(~rst)
       begin
               state=s0
               ;end
       else
               state=next_state;
end
always @(*)
begin
       case(state)
               s0:
               begin
                       if(synin==0)
                       begin
                               next_state=s0
                               ;out=0;
                               end
                       else
                       begin
                               next_state=s1
                               ;out=1;
                               end
               end
               s1:
               begin
```

```
if(synin==1)
                       begin
                               next_state=s1
                               ;out=0;
end
endcase
end
end else begin
end
next_state=s0;out=0;
endmodule
//designing the synchronizer
module synchron(in, clk, rst,synin);
input in,clk,rst;
output synin;
wire out;
D_FF ff1(out,in,clk,rst);
D_FF ff2(synin,out,clk,rst);
endmodule
//designing the D flipflop
module D_FF (q, d, clock, reset);
        output q;
        input d, clock,
        reset;reg q;
        always @(posedge clock)
        begin
               if (~reset)
                       q = 1'b0;
               els
                       q = d;
       end
endmodule
//designing the clock divider
module CLOCK_Divider(input CLK_100MHz,input RESET,output reg CLK_1hz);
        integer c=0;
        always @(posedge CLK_100MHz)
        begin
               if(~RESET)
               begin
```

end else c = 0; CLK_1hz=1; begin

CLK_1hz = ~CLK_1hz; c=0;

end

