

University of Engineering and Technology, Peshawar

Department of Computer Systems Engineering.

Course Lab: CSE-308 Digital System Design

Zubair Khan

Section

Batch

Submitted to



19 PWCSE 1797

A

21 (Spring_2022)

Engr. Madiha Sher

LAB 06 Title

4-Digit BCD Counter on Multiplexed Seven Segment Display


Objectives(s):

This lab will enable students to:

- Learn top down and bottom up design methodologies
- Learn to use time multiplexed 4-digit Seven Segment display


Theory

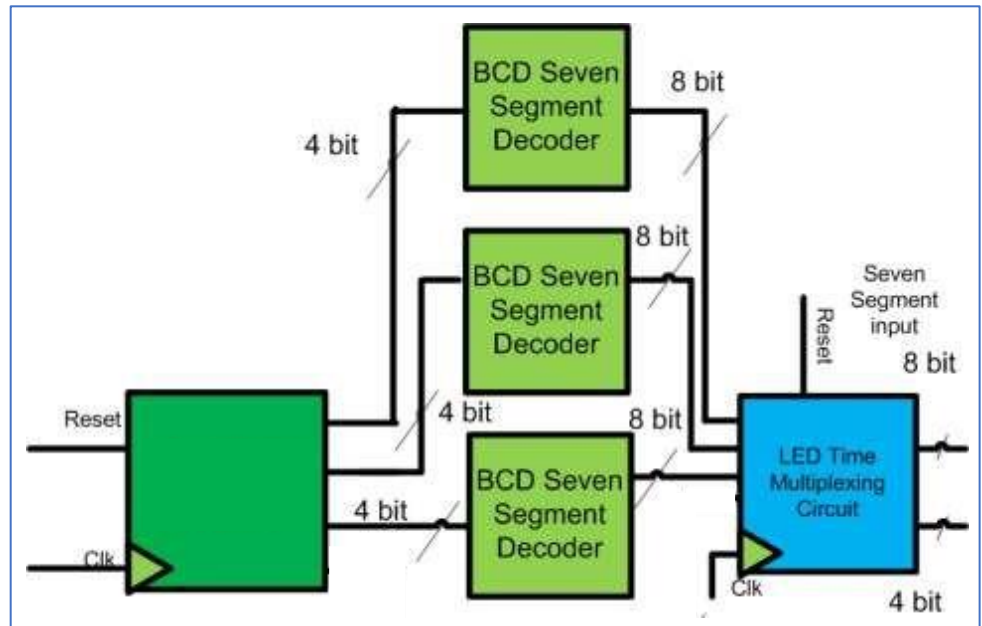Block Diagram: The S6 board has four seven-segment LED displays, each containing seven bars and one small round dot. To reduce the use of FPGA's I/O pins, the S6 board uses a time-multiplexing sharing scheme. In this scheme, the three displays have their individual enable signals but share eight common




signals to light the segments. All signals are active low (i.e., enabled when a signal is 0). The schematic of displaying a "2" on the leftmost LED is shown in Figure.

Note that the enable signal (i.e., an) is "011". This configuration clearly can enable only one display at a time. We can time-multiplex the four LED patterns by enabling the four displays in turn, as shown in the simplified timing diagram. If the refreshing rate of the enable signal is fast enough, the human eye cannot distinguish the on and off intervals of the LEDs and perceives that all four displays are lit simultaneously. This scheme reduces the number of I/O pins from 32 to 11 (i.e., eight LED segments plus three enable signals) but requires a time-multiplexing circuit.

 

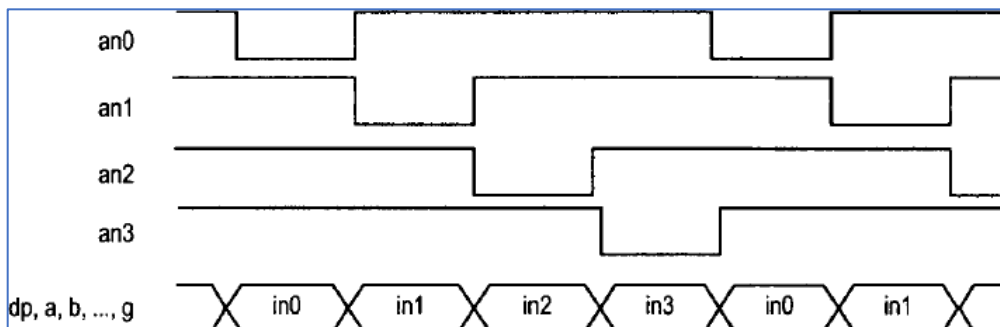3 Digit BCD Counter and timing diagram of LED multiplexing



LED time Multiplexing

The refresh rate of the enable signal has to be fast enough to fool our eyes but should be slow enough so that the LEDs can be turned on and off completely. The rate around the range 1000 Hz should work properly. In our design, we use an 18-bit binary counter for this purpose. The two MSBs are decoded to generate the enable signal and are used as the selection signal for multiplexing

LAB TASK

Implement a BCD counter that runs from 000 to 999 and shows each BCD digit on the seven-segment display.

Explanation:

In this LAB we have don two tasks 6a and 6b

- **6a:** Implementation of BCD counter that runs from 0 to 9 and shows each BCD digit on the seven-segment display
- **6b:** Implementation of BCD counter that runs from 000 to 999 and shows each BCD digit on the seven-segment display

6a: Implementation of BCD counter that runs from 0 to 9 and shows each BCD digit on the seven-segment display

Source Code

For [*.v] file (Verilog)

```
module counter(  
    input clk, rst,  
    output [2:0]en,  
    output [6:0] counter7seg  
);  
    reg [3:0] counter;  
    assign en = 3'b011;  
  
    seven_seg seg(counter, counter7seg);  
    clk_divider Div_Clock(clk, clk1, rst);  
  
    always @ (posedge clk1)  
    begin  
        if(rst)  
            counter = 0;  
        else  
            begin  
                counter = counter + 1'b1;  
                if(counter == 10)  
                    counter = 0;  
            end  
        end  
    end  
endmodule  
  
module seven_seg(  
    input [3:0] in,  
    output [6:0] out  
);  
    assign out = (in == 0) ? 7'd0:  
                (in == 1) ? 7'b11111001:  
                (in == 2) ? 7'b0100100:  
                (in == 3) ? 7'b0110000:  
                (in == 4) ? 7'b0011001:  
                (in == 5) ? 7'b0010010:  
                (in == 6) ? 7'b0000010;
```

```

        (in == 7) ? 7'b11111000:
        (in == 8) ? 7'b00000000:
        (in == 9) ? 7'b00111000: 7'b11111111;
endmodule

module clk_divider(clk, clk1, rst);
    integer cnt;
    input clk, rst;
    output reg clk1;
    always @(posedge clk)
        begin
            if(rst)
                begin
                    cnt = 0;
                    clk1 = 0;
                end
            else
                begin
                    cnt = cnt + 1;
                    if(cnt == 10000000)
                        begin
                            clk1 = ~clk1;
                            cnt = 0;
                        end
                end
            end
        end
endmodule

```

6b: Implementation of BCD counter that runs from 000 to 999 and shows each BCD digit on the seven-segment display

Source Code

For [*.v] file (verilog)

```
module counter(  
    input clk, rst,  
    output [2:0]en,  
    output [6:0] counter7seg  
);  
  
    reg [3:0] U,T,H;  
  
    seven_seg seg_7(U,T,H, en, clk, rst, counter7seg);  
    clk_divider Div_Clock(clk, clk1, rst);  
  
    always @ (posedge clk1)  
    if(rst)  
    begin  
        U = 0;  
        T = 0;  
        H = 0;  
    end  
    else  
    begin  
        U = U + 1'b1;  
        if(U == 10)  
        begin  
            U = 0;  
            T = T + 1'b1;  
            if(T == 10)  
            begin  
                T = 0;  
                H = H + 1'b1;  
                if(H==10)  
                H = 0;  
            end  
        end  
    end  
end  
  
endmodule
```

```

module seven_seg(U,T,H, en, clk, rst, out);
input [3:0]U,T,H;
output reg [2:0]en;
input clk,rst;
output [6:0]out;
reg[3:0]in;
    assign out = (in == 0) ? 7'd0:
                  (in == 1) ? 7'b1111001:
                  (in == 2) ? 7'b0100100:
                  (in == 3) ? 7'b0110000:
                  (in == 4) ? 7'b0011001:
                  (in == 5) ? 7'b0010010:
                  (in == 6) ? 7'b0000010:
                  (in == 7) ? 7'b1111000:
                  (in == 8) ? 7'b0000000:
                  (in == 9) ? 7'b0011000: 7'b1111111;

    always @(posedge clk)
    begin
        if(rst)
            in = U;
        else begin
            if(en == 3'b110) begin
                en = 3'b101;
                in = T;
            end
            else begin
                if(en == 3'b101)begin
                    en = 3'b 011;
                    in = H;
                end
            end
        end
    end
end
endmodule

```

```

module clk_divider(clk, clk1, rst);
integer cnt;
input clk, rst;
output reg clk1;
always @(posedge clk)
begin
    if(rst)
        begin
            cnt = 0;

```

```

        clk1 = 0;
    end
else
    begin
        cnt = cnt + 1;
        if(cnt == 100000000)
            begin
                clk1 = ~clk1;
                cnt = 0;
            end
        end
    end
end
endmodule

```

For [*.ucf] file (verilog)

```

NET "clk" LOC = V10;
NET "rst" LOC = F17;
NET "en[2]" LOC = B3;
NET "en[1]" LOC = A2;
NET "en[0]" LOC = B2;
NET "counter7seg[6]" LOC = A3;
NET "counter7seg[5]" LOC = B4;
NET "counter7seg[4]" LOC = A4;
NET "counter7seg[3]" LOC = C4;
NET "counter7seg[2]" LOC = C5;
NET "counter7seg[1]" LOC = D6;
NET "counter7seg[0]" LOC = A5;
NET "counter7seg[6]" SLEW = FAST;
NET "counter7seg[5]" SLEW = FAST;
NET "counter7seg[4]" SLEW = FAST;
NET "counter7seg[3]" SLEW = FAST;
NET "counter7seg[2]" SLEW = FAST;
NET "counter7seg[1]" SLEW = FAST;
NET "counter7seg[0]" SLEW = FAST;
# PlanAhead Generated IO constraints

NET "en[2]" SLEW = FAST;
NET "en[1]" SLEW = FAST;
NET "en[0]" SLEW = FAST;

```