

University of Engineering and Technology, Peshawar

Department of Computer Systems Engineering.

Course Lab: CSE-308 Digital System Design

Zubair Khan

Section

Batch

Submitted to



19 PWCSE 1797

A

21 (Spring_2022)

Engr. Madiha Sher

LAB # 9 TITLE

IMPLEMENT A TRAFFIC LIGHT CONTROLLER USING FSM.

INTRODUCTION:

The lab this week will continue the introduction to FSMs with a simple Traffic Light Controller design project. In the lab, you are required to create a state diagram of a Mealy machine, which implements a traffic light controller, based on provided guidelines. You will then use this state diagram to write the behavioral Verilog description of the traffic light controller. The testing of your traffic light controller will take place during the lab session using the ISE development tools and the Spartan 6 board. As with the previous lab, we will make use of the character LEDs to display the outputs of our digital circuit.

THE TRAFFIC LIGHT CONTROLLER:

This week you will design a traffic light controller for the highway and farm road intersection shown in Figure 1. For simplicity, we will assume that the traffic lights on opposite ends of the intersection are the same; in other words, if the light for the North bound traffic is green, then the light for the South bound traffic is also green. The traffic light controller outputs two 2-bit signals, highwaySignal and farmSignal, for the highway road and the farm road, respectively.

 


Figure 1: Example Illustration

The following encoding is used for both signals:

001 : Green

010 : Yellow

100 : Red

Obviously, to avoid accidents, the highway lights and farm road lights must not be green at the same time. Furthermore, the transitions from green on each road must be followed by 3 seconds of yellow. Because the traffic on the highway is much greater than that of the farm road, the traffic light must remain green on the highway longer than on the farm road. For this design, the highway light must remain green unless there is a vehicle on the farm road, while the farm road light must remain green for only 10 seconds.

The brain of the traffic light controller is the FSM. For the initial design, Vehicle, Clock and Rst constitute the only input to the FSM. The output of the FSM includes the highwaySignal and farmSignal. The operation of the FSM can be described by using a state diagram as shown in figure 2.

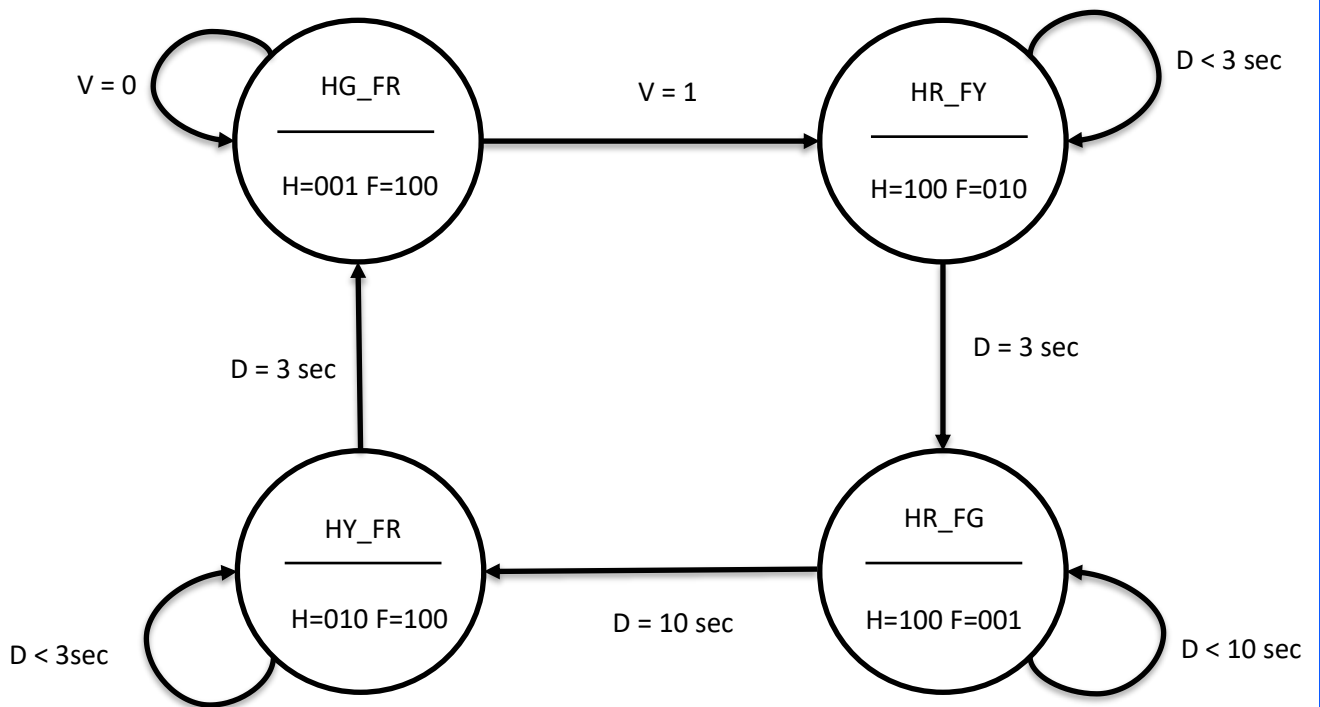


Figure 2: State Transition Diagram

CODE:

```
module D_FF (q, d, clock, reset);
```

```

output reg q;
input d, clock, reset;
always @(negedge clock or posedge reset)
begin
    if (reset)
        q = 1'b0;
    else
        q = d;
end
endmodule

```

```

module synchronizer(
    input clk, rst, in,
    output out
);
    wire w1;
    D_FF DF01 (w1, in, clk, rst);
    D_FF DF02 (out, w1, clk, rst);
endmodule

```

```

module clk_divider(clk, clk1, rst);
    integer cnt;
    input clk, rst;
    output reg clk1;
    always @(posedge clk)
        begin
            if(rst)
                begin
                    cnt = 0;
                    clk1 = 0;
                end
            else
                begin
                    cnt = cnt + 1;

```

```

                                if(cnt == 100000000)
                                    begin
                                        clk1 = ~clk1;
                                        cnt = 0;
                                    end
                                end
                            end
endmodule

```

```

module L2P(
    input clk1, rst, in,
    output reg out
);

    synchronizer sync (clk1, rst, in, synin);

    parameter s0 = 0;
    parameter s1 = 1;

    reg state;
    reg next_state;

    always @(posedge clk1)
        if(rst)
            begin
                state = s0;
            end
        else
            state = next_state;

    always @(*) begin

        case (state)
        s0:
            begin
                if(synin == 0)
                    begin

```

```

        out = 0;
        next_state = s0;
    end
    else if(synin== 1)
    begin
        out = 1;
        next_state = s1;
    end
end
s1:
begin
    if(synin== 0)
    begin
        out = 0;
        next_state = s0;
    end
    else if(synin == 1)
    begin
        out = 0;
        next_state = s1;
    end
end

end

endcase
end
endmodule

```

```
//module lock (on, off, reset,clk,onpulse,offpulse, out);
```

```
module traffic_controller(reset, clk, VEHICAL_IN, HighWayLight, FarmLight,state7seg,enable);
```

```

input reset, VEHICAL_IN, clk;
output reg [2:0] HighWayLight, FarmLight;
    output [6:0] state7seg;
    output enable;

```



```

        end
    end

    FY_HR:
        begin
            FarmLight = YELLOW;
            HighWayLight = RED;
            next_state = FG_HR;
        end

    FG_HR:
        begin
            FarmLight = GREEN;
            HighWayLight = RED;
            next_state = FR_HY;
        end

    FR_HY:
        begin
            FarmLight = RED;
            HighWayLight = YELLOW;
            next_state = FR_HG;
        end
    endcase
end
endmodule

```

```

module seven_seg(in, out);
    input [1:0] in;
    output [6:0] out;
    assign out = (in == 0) ? 7'b1000000:
                    (in == 1) ? 7'b1111001:
                    (in == 2) ? 7'b0100100:
                    (in == 3) ? 7'b0110000: 7'b1111111;
endmodule

```



```

// module seven_seg(in, out);
//   input [1:0] in;
//   output [6:0] out;
//   assign out = (in == 0) ? 7'd0:
//               (in == 1) ? 7'b1111001:
//               (in == 2) ? 7'b0100100:
//               (in == 3) ? 7'b0110000:
//               (in == 4) ? 7'b0011001:
//               (in == 5) ? 7'b0010010:
//               (in == 6) ? 7'b0000010:
//               (in == 7) ? 7'b1111000:
//               (in == 8) ? 7'b0000000:
//               (in == 9) ? 7'b0011000: 7'b1111111;
// endmodule

```

UCF FILE:

```
//reset, clk, VEHICAL_IN, HighWayLight, FarmLight,state7seg
```

```

NET "reset" LOC = C17 | PULLUP;
NET "clk" LOC = V10 | PULLUP;
NET "VEHICAL_IN" LOC = F17 | PULLUP;

```

```

NET "HighWayLight[0]" LOC = P15;
NET "HighWayLight[1]" LOC = P16;
NET "HighWayLight[2]" LOC = N15;

```

```

NET "FarmLight[0]" LOC = N16;
NET "FarmLight[1]" LOC = U17;
NET "FarmLight[2]" LOC = U18;

```

```

NET "state7seg[0]" LOC = A3;
NET "state7seg[1]" LOC = B4;
NET "state7seg[2]" LOC = A4;
NET "state7seg[3]" LOC = C4;
NET "state7seg[4]" LOC = C5;

```

NET "state7seg[5]" LOC = D6;
NET "state7seg[6]" LOC = C6;

NET "enable" LOC = B3;

I/O PIN PLANNING:

Ports					
Name	Direction	Neg Diff Pair	Site	Fixed	B
All ports (17)					
FarmLight (3)	Output				
FarmLight[2]	Output		U18	<input checked="" type="checkbox"/>	
FarmLight[1]	Output		U17	<input checked="" type="checkbox"/>	
FarmLight[0]	Output		N16	<input checked="" type="checkbox"/>	
HighWayLight (3)	Output				
HighWayLight[2]	Output		N15	<input checked="" type="checkbox"/>	
HighWayLight[1]	Output		P16	<input checked="" type="checkbox"/>	
HighWayLight[0]	Output		P15	<input checked="" type="checkbox"/>	
state7seg (7)	Output				
state7seg[6]	Output		C6	<input checked="" type="checkbox"/>	
state7seg[5]	Output		D6	<input checked="" type="checkbox"/>	
state7seg[4]	Output		C5	<input checked="" type="checkbox"/>	
state7seg[3]	Output		C4	<input checked="" type="checkbox"/>	
state7seg[2]	Output		A4	<input checked="" type="checkbox"/>	
state7seg[1]	Output		B4	<input checked="" type="checkbox"/>	
state7seg[0]	Output		A3	<input checked="" type="checkbox"/>	
Scalar ports (4)					
clk	Input		V10	<input checked="" type="checkbox"/>	
enable	Output		B3	<input checked="" type="checkbox"/>	
reset	Input		C17	<input checked="" type="checkbox"/>	
VEHICAL_IN	Input		F17	<input checked="" type="checkbox"/>	

OUTPUT:

