

# University of Engineering and Technology, Peshawar

Department of Computer Systems Engineering.

Course Lab: CSE-308 Digital System Design

Zubair Khan

Section

Batch

Submitted to



19 PWCSE 1797

A

21 (Spring\_2022)

Engr. Madiha Sher

## LAB # 5 TITLE

### IMPLEMENTATION OF A 8 BIT RING COUNTER


#### Objective:

- To become familiarized with behavior level modeling
- To be able to implement sequential circuits using Verilog
- To Implement an 8 Bit Ring Counter on Spartan 6 FPGA starter kit.
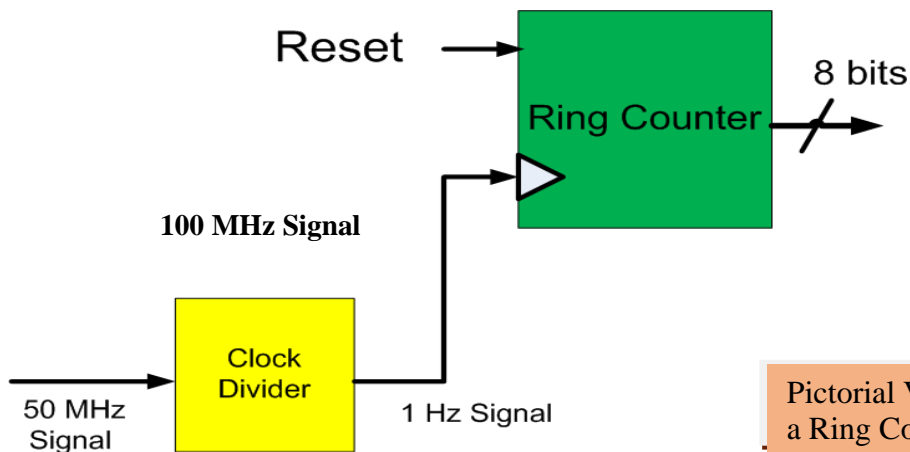
### Block Diagram:

The Spartan 6 kit has a clock source of 100 MHz. If we use it in applications like counters, the counter will count at an incredibly fast speed and we will not be able to see the output. Your task is to divide the 100 MHz frequency into a 1 Hz frequency. The Module Clock divider is responsible for it.

The functional detail of the 8-bit Ring Counter is shown in the following figures.



Pictorial View of the Operation of a Ring Counter

count [7:0]							
0	0	0	0	0	0	0	1
0	0	0	0	0	0	1	0
0	0	0	0	0	1	0	0
0	0	0	0	1	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	1	0	0	0	0	0	0
1	0	0	0	0	0	0	0
0	0	0	0	0	0	0	1

### I/O Connection:

The output of the Ring Counter should be connected to 8 LEDs on Spartan 3 Starter Kit. The clock input is connected to pin “T9” on the board. The LEDs should turn on and off one by one from left to Right with an interval of 1 second.

### CODE:

```
module ringcounter(  
    input  clk,  
    input  rst,  
    output reg [7:0] count  
    //reg [7:0] count  
);  
  
clk_divider cd(clk,clk1,rst);  
always @(posedge clk1)  
begin  
    if(rst)  
        count<=8'b10000000;  
    else  
        begin  
            count <= count << 1; //Shift Left (Fill with Zero)  
            count[0] <= count[7];  
            //Compare blocking assignment (=) VS non-blocking assignment (<=)  
        end  
    end  
end  
  
endmodule  
  
module clk_divider(clk,clk1,rst);  
integer counter=0;  
input clk,rst;  
output reg clk1;  
always@(posedge clk)  
begin  
    if(rst)  
        begin  
            counter=0;  
            clk1=0;  
        end  
    else  
        begin  
            counter=counter+1;  
            if(counter==1000000)  
                begin  
                    clk1=~clk1;  
                    counter=0;  
                end  
            end  
        end  
    end  
end  
endmodule
```

### UCF FILE:

## # PlanAhead Generated physical constraints

```
NET "clk" LOC = V10;  
NET "rst" LOC = F17;  
NET "count[0]" LOC = P15;  
NET "count[1]" LOC = P16;  
NET "count[2]" LOC = N15;  
NET "count[3]" LOC = N16;  
NET "count[4]" LOC = U17;  
NET "count[5]" LOC = U18;  
NET "count[6]" LOC = T17;  
NET "count[7]" LOC = T18;
```

## I/O PIN PLANNING:

I/O Ports											
Name	Direction	Neg Diff Pair	Site	Fixed	Bank	I/O Std	Vcco	Vref	Drive Stre...	Slew T... ^1	Pull Type
All ports (10)											
Scalar ports (2)											
clk	Input		V10	<input checked="" type="checkbox"/>		2 default (LVCMOS25)					NONE
rst	Input		F17	<input checked="" type="checkbox"/>		1 default (LVCMOS25)					NONE
count (8)											
count[7]	Output		T18	<input checked="" type="checkbox"/>		1 default (LVCMOS25)	2.500		12 SLOW		NONE
count[6]	Output		T17	<input checked="" type="checkbox"/>		1 default (LVCMOS25)	2.500		12 SLOW		NONE
count[5]	Output		U18	<input checked="" type="checkbox"/>		1 default (LVCMOS25)	2.500		12 SLOW		NONE
count[4]	Output		U17	<input checked="" type="checkbox"/>		1 default (LVCMOS25)	2.500		12 SLOW		NONE
count[3]	Output		N16	<input checked="" type="checkbox"/>		1 default (LVCMOS25)	2.500		12 SLOW		NONE
count[2]	Output		N15	<input checked="" type="checkbox"/>		1 default (LVCMOS25)	2.500		12 SLOW		NONE
count[1]	Output		P16	<input checked="" type="checkbox"/>		1 default (LVCMOS25)	2.500		12 SLOW		NONE
count[0]	Output		P15	<input checked="" type="checkbox"/>		1 default (LVCMOS25)	2.500		12 SLOW		NONE

## OUTPUT:

