

# University of Engineering and Technology, Peshawar

Department of Computer Systems Engineering.

Course Lab: CSE-308 Digital System Design

**Zubair Khan**

Section

Batch

Submitted to



**19 PWCSE 1797**

**A**

21 (Spring\_2022)

Engr. Madiha Sher

## **LAB # 4 TITLE**

### **BCD TO SEVEN SEGMENT DECODER**


#### *Objective:*

*To implement a BCD to Seven Segment Decoder on Spartan 6 board.*
 
## Block Diagram:

In This lab you are required to take a BCD input from the user and display that number on the seven segment display. Following diagram shows the 7 bit code for displaying “2” on the seven segment display all the input are active low signals. Note that enable signal should be held low in order to turn on the particular seven segment display. There are 4 seven segment displays on the Spartan 6 board. In later labs you will learn how to use time multiplexing techniques to turn on all the four seven segment displays as the input A,B,C,D,E,F,G, Dp are shared by all the four seven segment displays.

**I/O Connections:** your module will have 4 bit input and 8 bit output. Connect input to switches and output to seven segment display.



## Lab Task:

- 1- Using switches enter a BCD number and show the resulting number on the seven segment display.

## Code:

```

////////////////////////////////////
module task1(
    output dp,
    input en,
    input [3:0] in,
    output [6:0] out
);

assign dp=en;
assign out=(in==0)?7'b1000000:
            (in==1)?7'b1111001:
            (in==2)?7'b0100100:
            (in==3)?7'b0110000:
            (in==4)?7'b0011001:
            (in==5)?7'b0010010:
            (in==6)?7'b0000010:
            (in==7)?7'b1111000:
            (in==8)?7'b0000000:
            (in==9)?7'b0010000:7'b1111111;

endmodule

```

UCF File:

```

1
2 NET "in[3]" PULLUP;
3 NET "in[2]" PULLUP;
4 NET "in[1]" PULLUP;
5 NET "in[0]" PULLUP;
6
7
8 NET "out[0]" LOC = A3;
9 NET "out[3]" LOC = C4;
10 NET "out[2]" LOC = A4;
11 NET "out[5]" LOC = D6;
12 NET "out[1]" LOC = B4;
13 NET "out[4]" LOC = C5;
14 NET "en" LOC = C17;
15 NET "dp" LOC = B3;
16 NET "in[3]" LOC = E18;
17
18
19 NET "out[6]" SLEW = FAST;
20 NET "out[5]" SLEW = FAST;
21 NET "out[4]" SLEW = FAST;
22 NET "out[3]" SLEW = FAST;
23 NET "out[2]" SLEW = FAST;
24 NET "out[1]" SLEW = FAST;
25 NET "out[0]" SLEW = FAST;

```

```

26
27
28 NET "out[6]" LOC = C6;
29
30
31 NET "dp" SLEW = FAST;
32 NET "en" PULLUP;
33
34
35 NET "in[2]" LOC = E16;
36 NET "in[1]" LOC = F18;
37 NET "in[0]" LOC = F17;
38

```

### I/O Pin Planning:


I/O Ports


Name	Direction	Neg Diff Pair	Site	Fixed	Bank	I/O Std	Vcco	Vref	Drive Stre...	Slew Type	Pull Type	Off-Chip T...	IN_TERM	OUT_TERM
All ports (13)														
in (4)														
in[3]	Input		E18	<input checked="" type="checkbox"/>		1 default (LVCMOS25)					PULLUP*	NONE	NONE	
in[2]	Input		E16	<input checked="" type="checkbox"/>		1 default (LVCMOS25)					PULLUP*	NONE	NONE	
in[1]	Input		F18	<input checked="" type="checkbox"/>		1 default (LVCMOS25)					PULLUP*	NONE	NONE	
in[0]	Input		F17	<input checked="" type="checkbox"/>		1 default (LVCMOS25)					PULLUP*	NONE	NONE	
out (7)														
out[6]	Output		C6	<input checked="" type="checkbox"/>		0 default (LVCMOS25)	2.500		12 FAST*		NONE	FP_VTT_50		NONE
out[5]	Output		D6	<input checked="" type="checkbox"/>		0 default (LVCMOS25)	2.500		12 FAST*		NONE	FP_VTT_50		NONE
out[4]	Output		C5	<input checked="" type="checkbox"/>		0 default (LVCMOS25)	2.500		12 FAST*		NONE	FP_VTT_50		NONE
out[3]	Output		C4	<input checked="" type="checkbox"/>		0 default (LVCMOS25)	2.500		12 FAST*		NONE	FP_VTT_50		NONE
out[2]	Output		A4	<input checked="" type="checkbox"/>		0 default (LVCMOS25)	2.500		12 FAST*		NONE	FP_VTT_50		NONE
out[1]	Output		B4	<input checked="" type="checkbox"/>		0 default (LVCMOS25)	2.500		12 FAST*		NONE	FP_VTT_50		NONE
out[0]	Output		A3	<input checked="" type="checkbox"/>		0 default (LVCMOS25)	2.500		12 FAST*		NONE	FP_VTT_50		NONE
Scalar ports (2)														
dp	Output		B3	<input checked="" type="checkbox"/>		0 default (LVCMOS25)	2.500		12 FAST*		NONE	FP_VTT_50		NONE
en	Input		C17	<input checked="" type="checkbox"/>		1 LVCMOS25					PULLUP*	NONE	NONE	

Td ConsolePackage PinsI/O Ports

Td ConsolePackage PinsI/O Ports

### Output:

 

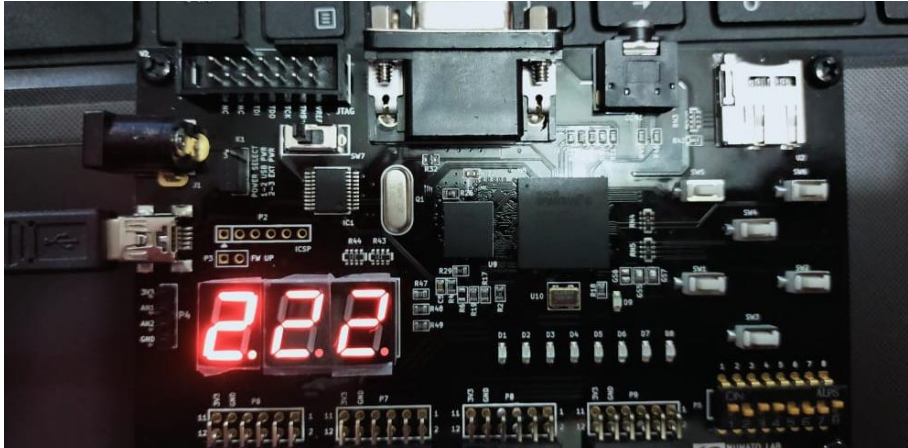


- 2- Connect the output of your lab 02 (4 bit adder) to the seven segment display. Note that number above 1001 are not valid BCD numbers. In this situation keep the seven segment display off and just the dp on.
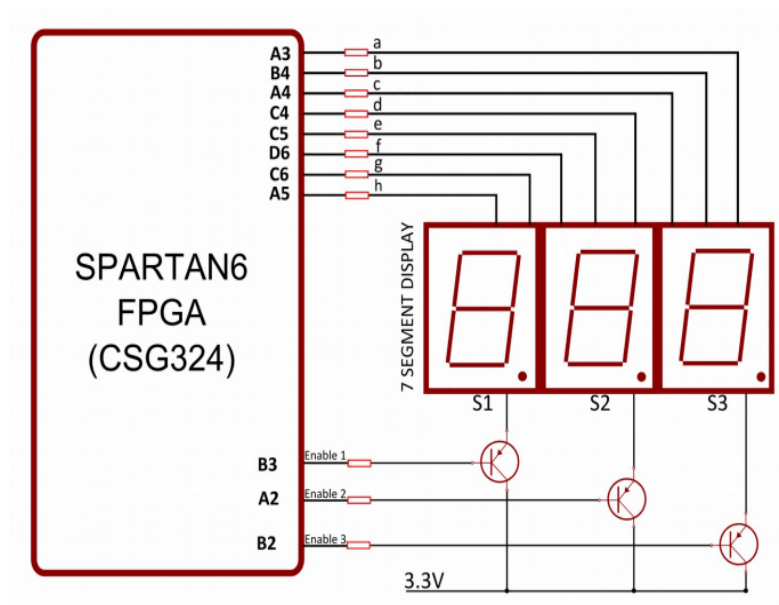
### 7 Segment Led Display On Spartan 6 Board

This board features three 7-segment LED display multiplexed for low pin count operation. Each module can be separately turned on and off with the three switching transistors.

Note: All signals (a, b, c, d, e, f, g, dot, enable 1, enable 2, enable 3) used for controlling 7-Segment display are active-low signals. So, for example, for displaying “8” in display-2, users need to drive Enable 2 to 0 as well as drive signals a, b, c, d, e, f to 0. All other signals need to be driven to 1.



Code:

```
module FullAdderr(Sum, Cout, X, Y, Cin);
input X, Y, Cin;
output Sum, Cout;
//Behavioural Code
assign {Cout,Sum}=X+Y+Cin;
endmodule

module RippleCarryAdder (Cout, S, X, Y);
output Cout;
output [3:0] S;
input [3:0] X, Y;
wire [2:0] C; //Intermediate/Internal Carries
// FA1 (Sum, Cout, X, Y, Cin); //FA1's Interface (I/O Pins)
FullAdderr fulla0 (S[0], C[0], X[0], Y[0], 1'b0);
FullAdderr fulla1 (S[1], C[1], X[1], Y[1], C[0]);
FullAdderr fulla2 (S[2], C[2], X[2], Y[2], C[1]);
FullAdderr fulla3 (S[3], Cout, X[3], Y[3], C[2]);
endmodule

module BCD_out(out,dp,en,Cout,X,Y);

output Cout;
wire [3:0] S;

input [3:0] X, Y;
RippleCarryAdder rcl(Cout,S,X,Y);
output [6:0] out;
output dp;
input en;

assign dp=en;
    assign out =
(S==0)?(7'b1000000):
(S==1)?(7'b1111001):
(S==2)?(7'b0100100):
(S==3)?(7'b0110000):
(S==4)?(7'b0011001):
(S==5)?(7'b0010010):
(S==6)?(7'b0000010):
(S==7)?(7'b1111000):
(S==8)?(7'b0000000):
(S==9)?(7'b0011000):(7'b1111111);

endmodule
```

UCF File:

```
# PlanAhead Generated IO constraints

NET "out[6]" SLEW = FAST;
NET "out[5]" SLEW = FAST;
NET "out[4]" SLEW = FAST;
NET "out[3]" SLEW = FAST;
NET "out[2]" SLEW = FAST;
NET "out[1]" SLEW = FAST;
NET "out[0]" SLEW = FAST;

# PlanAhead Generated physical constraints

NET "out[6]" LOC = C6;
NET "out[5]" LOC = D6;
NET "out[4]" LOC = C5;
NET "out[3]" LOC = C4;
NET "out[2]" LOC = A4;
NET "out[1]" LOC = B4;
NET "out[0]" LOC = A3;
NET "dp" LOC = B3;

# PlanAhead Generated IO constraints

NET "X[3]" PULLUP;
NET "X[2]" PULLUP;
NET "X[1]" PULLUP;

NET "X[0]" PULLUP;
NET "Y[3]" PULLUP;
NET "Y[2]" PULLUP;
NET "Y[1]" PULLUP;
NET "Y[0]" PULLUP;

# PlanAhead Generated physical constraints

NET "Cout" LOC = T18;
NET "en" LOC = M18;
NET "Y[3]" LOC = D18;
NET "Y[2]" LOC = D17;
NET "Y[1]" LOC = C18;
NET "Y[0]" LOC = C17;
NET "X[3]" LOC = F17;
NET "X[2]" LOC = F18;
NET "X[1]" LOC = E16;
NET "X[0]" LOC = E18;

# PlanAhead Generated IO constraints

NET "en" PULLUP;
```

## I/O Pin Planning:

I/O Ports														
Name	Direction	Neg Diff Pair	Site	Fixed	Bank	I/O Std	Vcco	Vref	Drive Stre...	Slew T...	Pull Type	Off-Chip T...	IN_TERM	OUT_TERM
All ports (18)														
out (7)	Output					0 default (LVCMOS25)	2.500		12 FAST*		NONE	FP_VTT_50		NONE
out[6]	Output		C6	<input checked="" type="checkbox"/>		0 default (LVCMOS25)	2.500		12 FAST*		NONE	FP_VTT_50		NONE
out[5]	Output		D6	<input checked="" type="checkbox"/>		0 default (LVCMOS25)	2.500		12 FAST*		NONE	FP_VTT_50		NONE
out[4]	Output		C5	<input checked="" type="checkbox"/>		0 default (LVCMOS25)	2.500		12 FAST*		NONE	FP_VTT_50		NONE
out[3]	Output		C4	<input checked="" type="checkbox"/>		0 default (LVCMOS25)	2.500		12 FAST*		NONE	FP_VTT_50		NONE
out[2]	Output		A4	<input checked="" type="checkbox"/>		0 default (LVCMOS25)	2.500		12 FAST*		NONE	FP_VTT_50		NONE
out[1]	Output		B4	<input checked="" type="checkbox"/>		0 default (LVCMOS25)	2.500		12 FAST*		NONE	FP_VTT_50		NONE
out[0]	Output		A3	<input checked="" type="checkbox"/>		0 default (LVCMOS25)	2.500		12 FAST*		NONE	FP_VTT_50		NONE
X (4)														
X[3]	Input		F17	<input checked="" type="checkbox"/>		1 default (LVCMOS25)					PULLUP*	NONE	NONE	
X[2]	Input		F18	<input checked="" type="checkbox"/>		1 default (LVCMOS25)					PULLUP*	NONE	NONE	
X[1]	Input		E16	<input checked="" type="checkbox"/>		1 default (LVCMOS25)					PULLUP*	NONE	NONE	
X[0]	Input		E18	<input checked="" type="checkbox"/>		1 default (LVCMOS25)					PULLUP*	NONE	NONE	
Y (4)														
Y[3]	Input		D18	<input checked="" type="checkbox"/>		1 default (LVCMOS25)					PULLUP*	NONE	NONE	
Y[2]	Input		D17	<input checked="" type="checkbox"/>		1 default (LVCMOS25)					PULLUP*	NONE	NONE	
Y[1]	Input		C18	<input checked="" type="checkbox"/>		1 default (LVCMOS25)					PULLUP*	NONE	NONE	
Y[0]	Input		C17	<input checked="" type="checkbox"/>		1 default (LVCMOS25)					PULLUP*	NONE	NONE	
Scalar ports (3)														
Cout	Output		T18	<input checked="" type="checkbox"/>		1 default (LVCMOS25)	2.500		12 SLOW		NONE	FP_VTT_50		NONE
dp	Output		B3	<input checked="" type="checkbox"/>		0 default (LVCMOS25)	2.500		12 SLOW		NONE	FP_VTT_50		NONE
en	Input		M18	<input checked="" type="checkbox"/>		1 default (LVCMOS25)					PULLUP*	NONE	NONE	